

# Lab Report

Batuhan Arslanoglu

May 2018

# Contents

<b>1</b>	<b>Theoretical part</b>	<b>2</b>
1.1	Circuit calculation . . . . .	2
1.2	Circuit diagram . . . . .	3
1.3	Circuit plot . . . . .	3
<b>2</b>	<b>Practical part</b>	<b>4</b>
2.1	Work with GEDA programs . . . . .	4
2.1.1	Work with gschem . . . . .	4
2.1.2	Work with gnetlist . . . . .	5
2.1.3	Work with ngspice . . . . .	6
2.2	Work with QUCS programs . . . . .	7


# Chapter 1

## Theoretical part


### 1.1 Circuit calculation

<b>R1</b>	10
<b>R2</b>	7
<b>V1</b>	0.96
<b>UR1</b>	0.56
<b>UR2</b>	0.39

## 1.2 Circuit diagram

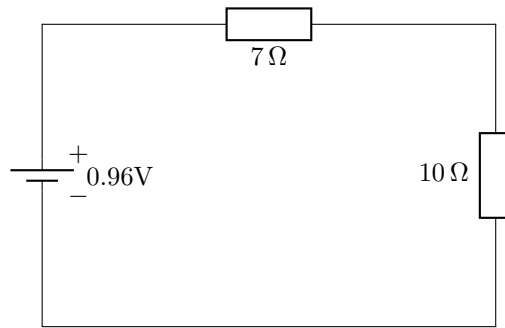

## 1.3 Circuit plot

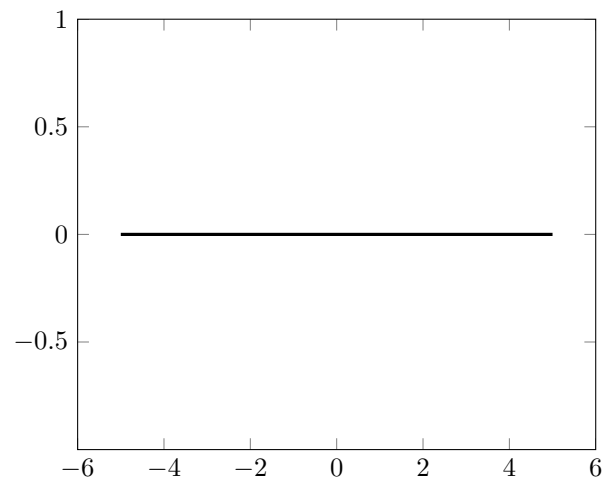

## Chapter 2

# Practical part

### 2.1 Work with GEDA programs

#### 2.1.1 Work with gschem

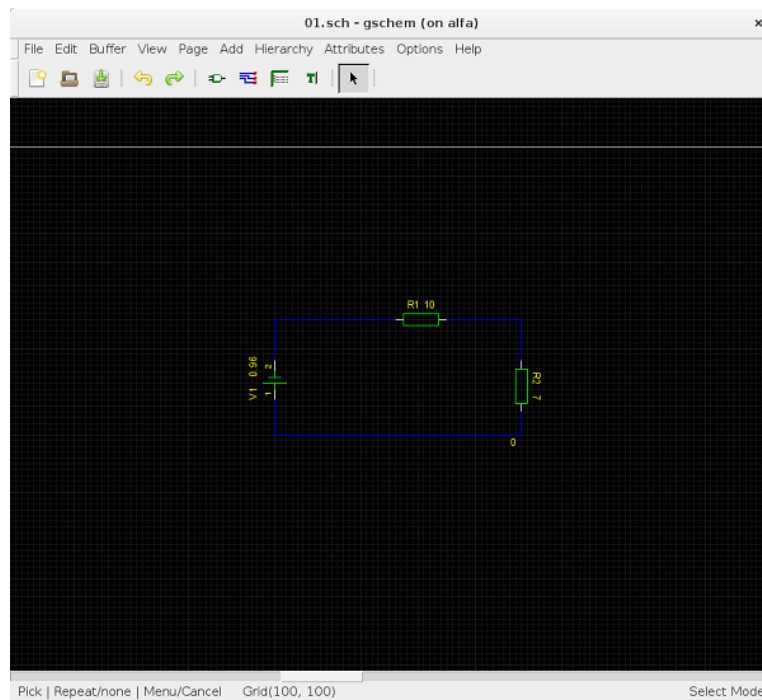


Figure 2.1: Circuit within the gEDA schematics environment.

### 2.1.2 Work with gnetlist

```
* Spice netlister for gnetlist
R2 2 0 7
R1 1 2 10
V1 0 1 0.96
.END
```

### 2.1.3 Work with ngspice

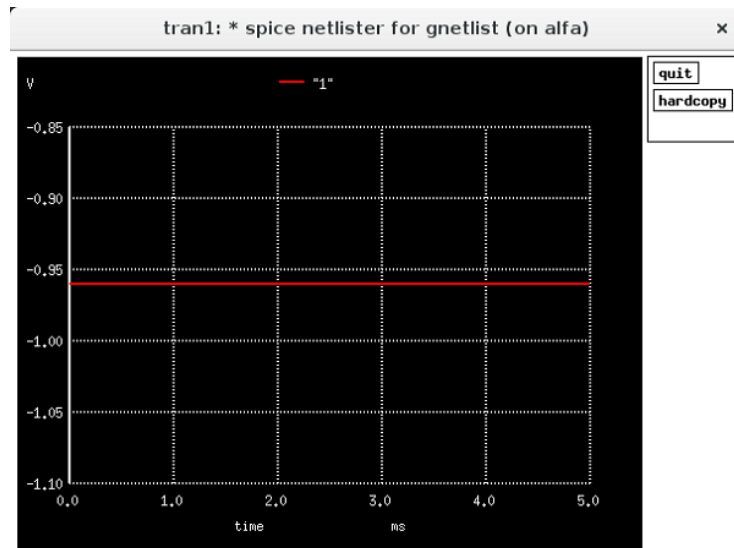


Figure 2.2: Simulation of voltage on resistor R1.

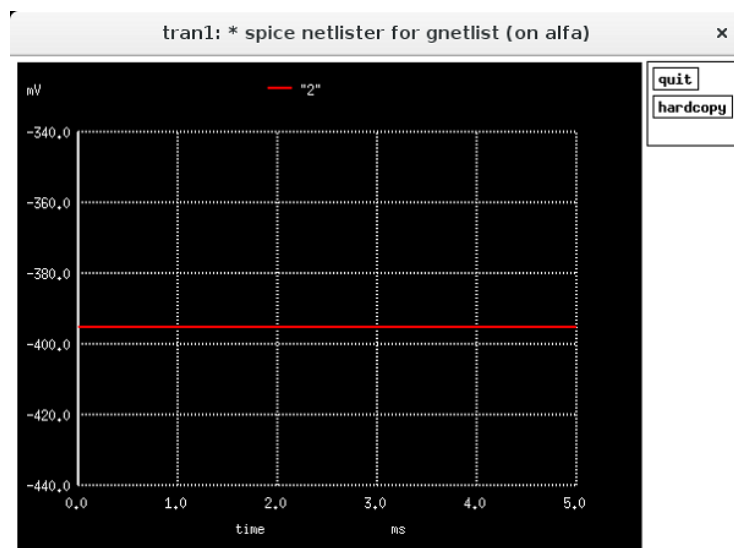


Figure 2.3: Simulation of voltage on resistor R2.

## 2.2 Work with QUCS programs

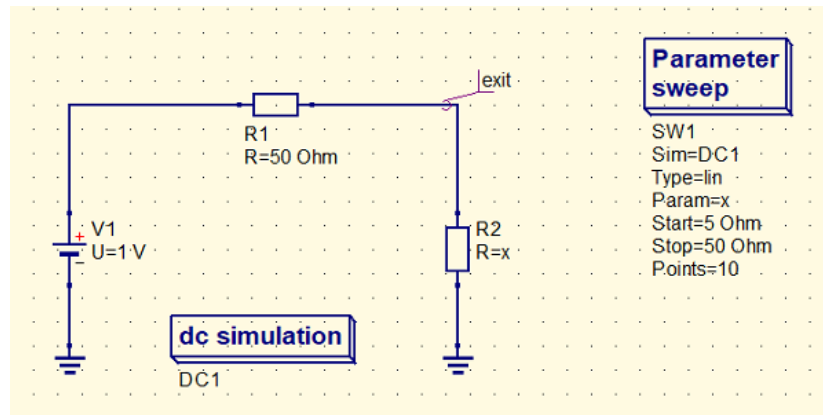


Figure 2.4: Circuit within the QUCS schematics environment.

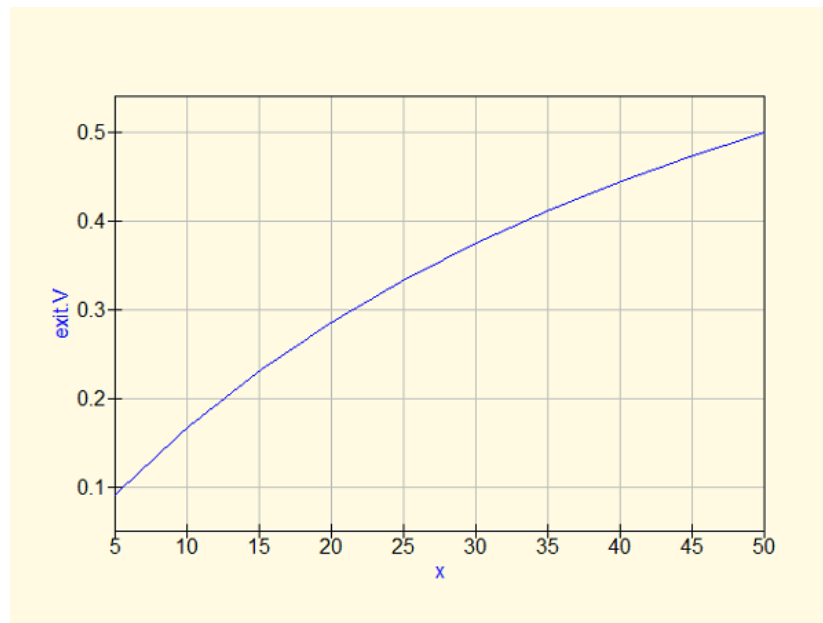


Figure 2.5: Plot with Cartesian coordinates, tabular view of currents flowing from points V1.1 and x.