

Lab Report

Batuhan Arslanoglu

May 2018

Contents

Chapter 1

Theoretical part

1.1 Circuit calculation

20pt	R1	10
	R2	7
	V1	0.96
	UR1	0.56
	UR2	0.39